```
1
     module normalLight (clk, reset, L, R, NL, NR, lightOn);
 2
         input logic clk, reset;
 3
         // L is true when left key is pressed, R is true when the right key
 4
         // is pressed, NL is true when the light on the left is on, and NR
 5
         // is true when the light on the right is on.
 6
         input logic L, R, NL, NR;
 7
         // when lightOn is true, the normal light should be on.
 8
         output logic lightOn;
9
         // Your code goes here!!
10
11
         enum {on, off} ps, ns;
12
13
         always comb begin
14
              case (ps)
15
                  on:
                         if(~R & L | R & ~L) ns = off;
16
                             else ns = on;
17
18
                  off:
                             if(NR & L & ~R | NL & R & ~L) ns = on;
19
                             else ns = off;
20
21
              endcase
22
         end
23
24
         always comb begin
25
              case (ps)
26
                  on: lightOn = 1;
27
28
                  off: lightOn = 0;
29
              endcase
30
         end
31
32
         always ff @(posedge clk) begin
33
              if(reset)
                  ps <= off;
34
35
              else
36
                  ps <= ns;
37
         end
38
     endmodule
39
40
     module normalLight testbench();
41
         logic clk, reset, L, R, NL, NR, lightOn;
42
43
         normalLight dut (.clk, .reset, .L, .R, .NL, .NR, .lightOn);
44
45
         parameter CLOCK PERIOD = 100;
46
         initial begin
47
              clk <= 0;
48
              forever #(CLOCK PERIOD / 2)
49
              clk <= ~clk;
50
         end
51
52
         initial begin
53
              reset <= 1; @(posedge clk);</pre>
54
              reset <= 0; @(posedge clk);</pre>
55
              L \le 0; R \le 0; NL \le 0; NR \le 0; repeat(4) @(posedge clk);
56
                                                 NR <= 1; repeat(4) @(posedge clk);</pre>
57
                                     NL <= 1; NR <= 0; repeat(4) @(posedge clk);
58
                                                  NR <= 1; repeat(4) @(posedge clk);</pre>
59
                         R \le 1; NL \le 0; NR \le 0; repeat(4) @(posedge clk);
60
                                                 NR <= 1; repeat(4) @(posedge clk);</pre>
61
                                     NL <= 1; NR <= 0; repeat(4) @(posedge clk);
62
                                                  NR <= 1; repeat(4) @(posedge clk);</pre>
63
              L \le 1; R \le 0; NL \le 0; NR \le 0; repeat(4) @(posedge clk);
64
                                                  NR <= 1; repeat(4) @(posedge clk);
65
                                     NL \le 1; NR \le 0; repeat(4) @(posedge clk);
66
                                                 NR <= 1; repeat(4) @(posedge clk);</pre>
67
                         R \le 1; NL \le 0; NR \le 0; repeat(4) @(posedge clk);
68
                                                  NR <= 1; repeat(4) @(posedge clk);</pre>
69
                                     NL \le 1; NR \le 0; repeat(4) @(posedge clk);
```

```
70
71 $stop;
72 end
73
74 endmodule
```

NR <= 1; repeat(4) @(posedge clk);</pre>